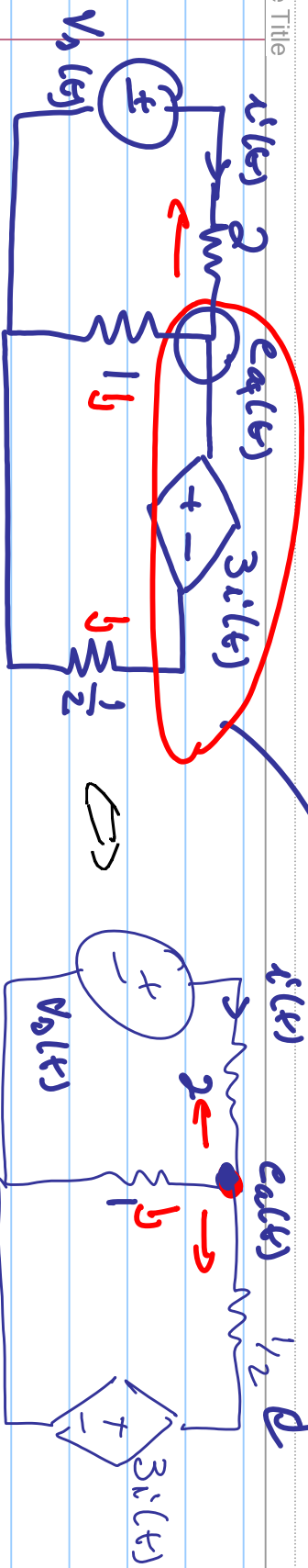


P 2.36

HW # 3



$$a) i(t) = \frac{V_0(t) - e_a(t)}{2}$$

$$b) \frac{e_a(t) - V_0(t)}{2} + \frac{e_a(t)}{1} + \frac{e_a(t) - 3i(t)}{1/2} = 0$$


$$\text{where } i(t) = \frac{V_0(t) - e_a(t)}{2}$$

$$\Rightarrow \frac{e_a(t) - V_0(t)}{2} + e_a(t) + 2e_a(t) - 3(V_0(t) - e_a(t)) = 0$$

$$\Rightarrow \frac{13}{2} e_a(t) = \frac{7}{2} V_0(t)$$

c)

p 2.37

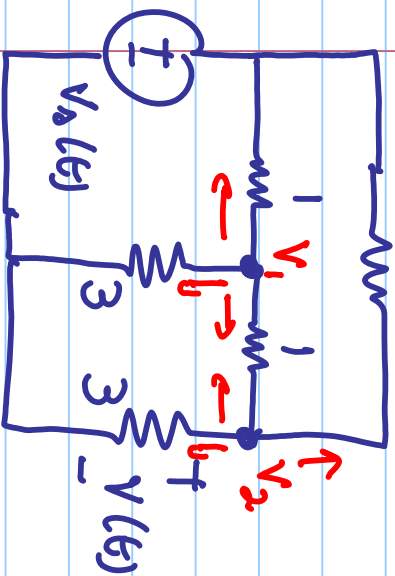

a) @ node V_1

$$\frac{V_1 - V_0}{1} + \frac{V_1}{3} + \frac{V_1 - V_2}{1} = 0$$

$$V_1(1 + 1 + 1/3) - V_2 = V_0$$

@ node V_2

$$\frac{V_2 - V_1}{1} + \frac{V_2 - V_0}{2} + \frac{V_2}{3} = 0$$

$$\Rightarrow -V_1 + V_2(1 + 1/2 + 1/3) = \frac{V_0}{2}$$

(2)

c) Solve for V_2 where $V_2 = V(t)$

$$\text{eq 1: } 7/3 V_1 = V_0 + V_2 \Rightarrow V_1 = \frac{3(V_0 - V_2)}{7}$$


Use eq 1 in eq 2 $\Rightarrow$

$$-3 \frac{(V_0 - V_2)}{7} + \frac{11}{6} V_2 = \frac{V_0}{2} \Rightarrow$$

$$V_2 \left(\frac{3}{7} + \frac{11}{6} \right) = \frac{V_0}{2} + \frac{3}{7} V_0 \Rightarrow$$

$$V_2(t) =$$

P 2-39

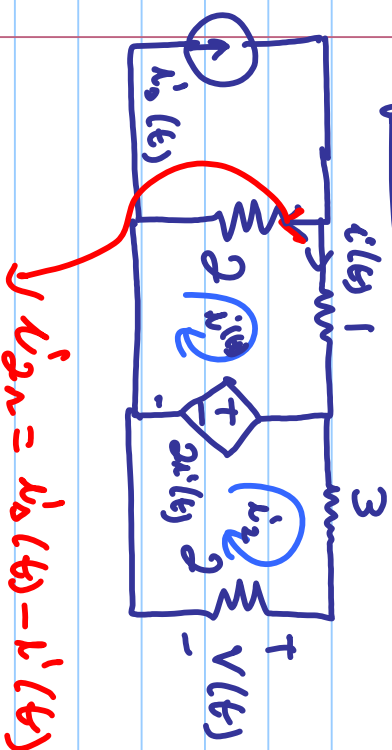

$$v(t) = 2i_1(t) \Rightarrow$$

$$v(t) = 2\left(-\frac{4}{5}\right)i_0(t)$$

$$\text{KVL: } 2(i_0(t) - i_1(t)) + 1(i_1(t)) + 2i_1(t) = 0$$

$$\Rightarrow 2i_0(t) - 2i_1(t) + i_1(t) + 2i_1(t) = 0$$


$$\Rightarrow i_1(t) = -2i_0(t) \quad (1)$$

$$\text{KVL 2: } -2i_1(t) + 3i_2(t) + 2i_2(t) = 0$$

$$\Rightarrow 5i_2(t) = 2i_1(t) \quad (2)$$

$$\text{Use eq 1 in 2} \Rightarrow 5i_2(t) = 2(-2i_0(t)) \Rightarrow i_2(t) = -\frac{4}{5}i_0(t)$$

P 2.42

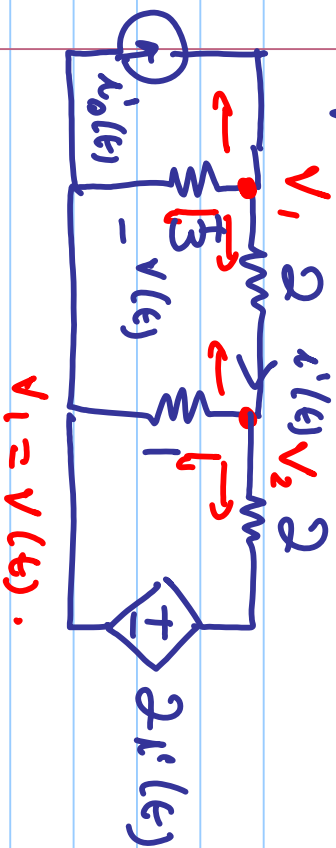

KCL @ V1

$$\frac{V_1}{3} + \frac{V_1 - V_2}{2} = u_0'(t)$$

$$V_1 \left(\frac{1}{3} + \frac{1}{2} \right) - \frac{V_2}{2} = u_0'(t)$$

$$V_1 \left(\frac{5}{6} \right) - \frac{1}{2} V_2 = u_0'(t)$$

$$\Rightarrow 5V_1 - 3V_2 = 6u_0'(t) \quad (1)$$

KCL @ V2

$$\frac{V_2 - V_1}{2} + \frac{V_2}{1} + \frac{V_2 - 2i'(t)}{2} = 0$$

Where $i'(t) = \frac{V_1 - V_2}{2} \Rightarrow$

$$\frac{V_2 - V_1}{2} + \frac{V_2}{1} + \frac{V_2 - V_1 + V_2}{2} = 0$$

$$-V_1 + \frac{5}{2} V_2 = 0 \Rightarrow -2V_1 + 5V_2 = 0$$

Replace eq. 2 into 1 $\Rightarrow$

$$5V_1 - 3 \left(\frac{2V_1}{5} \right) = 6u_0'(t) \Rightarrow$$


$$5V_1 - \frac{6}{5} V_1 = 6u_0'(t) \Rightarrow$$

$$25V_1 - 6V_1 = 30u_0'(t) \Rightarrow$$

$$19V_1 = 30u_0'(t) \Rightarrow$$

[Redacted]

P 2.44

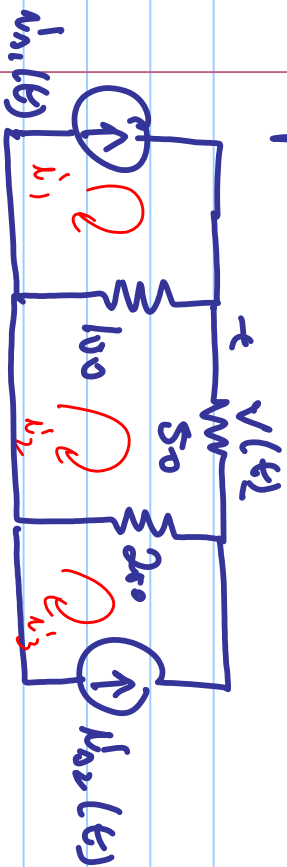

a) mesh will need one loop KVL.
nodal " " two KCL

b) loop analysis.

$$100(i_2 - i_1) + 50i_2 + 200(i_2 - i_3) = 0$$

$$\underline{500i_1 - 1000i_2}$$

$$-100i_1 + 350i_2 - 200i_3 = 0 \Rightarrow$$

$$=$$

$$350i_2 = 200i_3 + 100i_1 \text{ where}$$

$$i_3 = -i_2 \text{ and } i_1 = i_2(t) \Rightarrow$$


$$350i_2 = 100i_1 - 200i_2$$

$$i_2(t) = \frac{100i_1 - 200i_2}{350}$$

$$\therefore V(t) = 50i_2(t) \Rightarrow$$

$$= 50 \left(\frac{100i_1 - 200i_2}{350} \right)$$

P 2.46

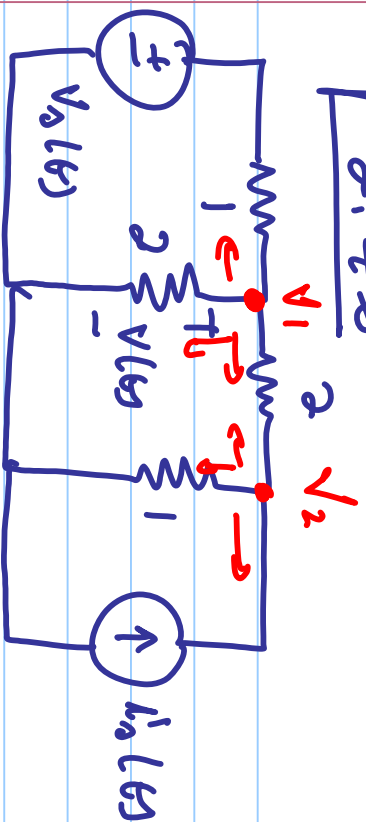

$$\text{eq 1: } V_2 = 4V_1 - 2V_0$$

$$\text{Use eq 1. into eq 2} \Rightarrow -V_1 + 3(4V_1 - 2V_0) = 2V_0 \Rightarrow$$

a) use nodal analysis.

$$11V_1 = 2V_0 + 6V_0 \Rightarrow$$


$$\text{eq 1} \quad \frac{V_1 - V_0}{1} + \frac{V_1}{2} + \frac{V_1 - V_2}{2} = 0$$

$$2V_1 - \frac{1}{2}V_2 = V_0 \Rightarrow 4V_1 - V_2 = 2V_0 \quad (1)$$

$$\text{eq 2} \quad \frac{V_2 - V_1}{2} + V_2 - V_0 = 0 \Rightarrow$$

$$-\frac{1}{2}V_1 + \frac{3}{2}V_2 = V_0 \Rightarrow -V_1 + 3V_2 = 2V_0 \quad (2)$$

2-60 a)

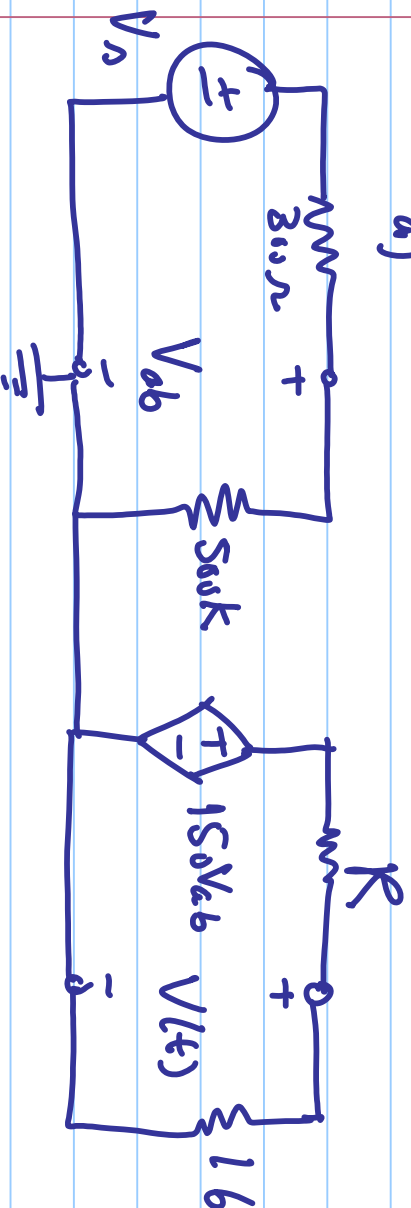

$$① V_{ab} = V_a \left(\frac{500,000}{500,000 + 300} \right) \Rightarrow V_{ab} \approx V_a$$

② Second half of the circuit $\Rightarrow$


$$V(t) = 150V_{ab} \left(\frac{16}{16 + R} \right) \Rightarrow \text{we know that } V_{ab} = V_a \Rightarrow$$

$$20 \cos(1000t) = 150 \times 0.2 \cos(1000t) \left(\frac{16}{16 + R} \right) \Rightarrow 20 = 30 \left(\frac{16}{16 + R} \right)$$

$$\Rightarrow \frac{2}{3} = \frac{16}{16+K} \Rightarrow 2(16+K) = 3 \times 16 = 48 \Rightarrow$$

$$32 + 2K = 48 \Rightarrow 2K = 48 - 32 = 16 = \text{[REDACTED]}$$

P 3.14

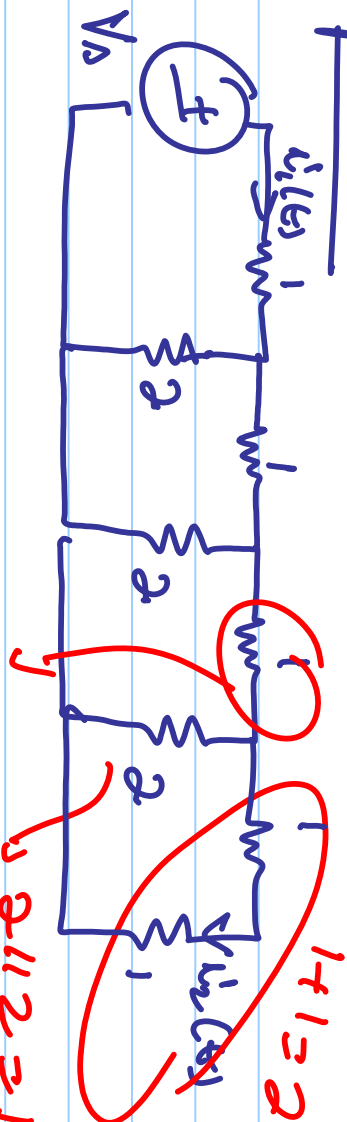


a)

$$\begin{aligned} 1+1 &= 2 & 2+1 &= 2 \\ 2+1 &= 1 & 1+1 &= 2 \\ 1+1 &= 2 & 2+1 &= 1 \end{aligned}$$

$$i_1(t) = \frac{V_0}{2} = \frac{1}{2} V_0(t)$$

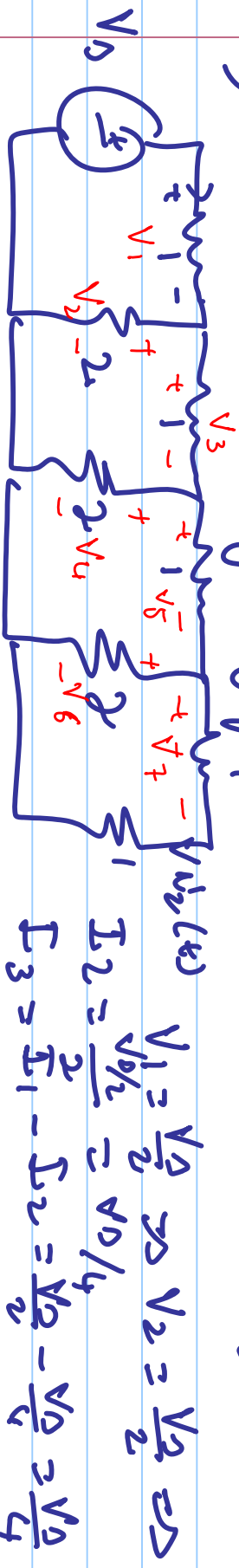b) take advantage of part a, we know $i_1(t) = \frac{V_0}{2} \Rightarrow V_{1,2} = \frac{V_0}{2}$



$$\begin{aligned} V_1 &= \frac{V_0}{2} \Rightarrow V_2 = \frac{V_0}{2} \Rightarrow \\ I_2 &= \frac{V_0/2}{2} = V_0/4 \\ I_3 &= I_1 - I_2 = \frac{V_0}{2} - \frac{V_0}{4} = \frac{V_0}{4} \end{aligned}$$

$$\Rightarrow V_3 = \frac{V_D}{4} \Rightarrow \therefore V_4 = V_2 - V_3 = \frac{V_D}{2} - \frac{V_D}{4} = \frac{V_D}{4}.$$


$$\Rightarrow I_4 = \frac{V_D}{8} \therefore I_5 = \frac{V_D}{4} - \frac{V_D}{8} = \frac{V_D}{8} \Rightarrow V_5 = \frac{V_D}{8}.$$

$$V_6 = V_4 - V_5 = \frac{V_D}{4} - \frac{V_D}{8} = \frac{V_D}{8} \Rightarrow I_6 = \frac{V_D}{16}$$

$$\Rightarrow I_7 = i_2 (A) = I_5 - I_6 = \frac{V_D}{8} - \frac{V_D}{16} = \frac{V_D}{16}$$

You can see the pattern after we calculate V_4 ; all voltages across are multiple of 2.



P 3.45 .

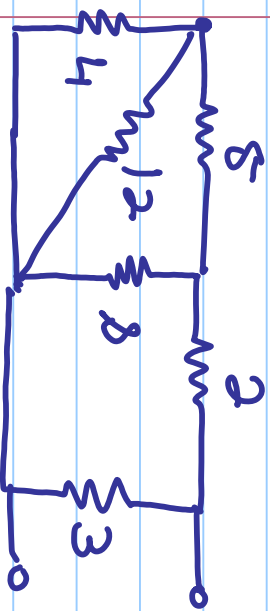

$$4 \parallel 12 = \frac{4 \times 12}{4 + 12} = \frac{48}{16} = 3$$

3 in series with 5 $\Rightarrow 3 + 5 = 8 \Omega$

$$8 \parallel 8 = 4$$

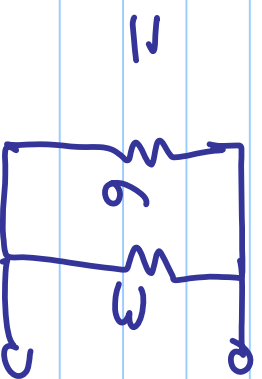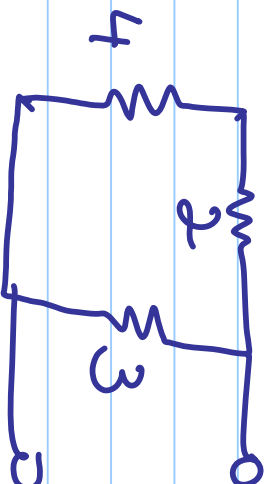

$\Rightarrow$



3.47

a) $10k \parallel 10k \Rightarrow 10 + 10 = 20k.$

b) $20 + 5 = 25k.$

c) $20 \parallel 10 = 6667\Omega.$