

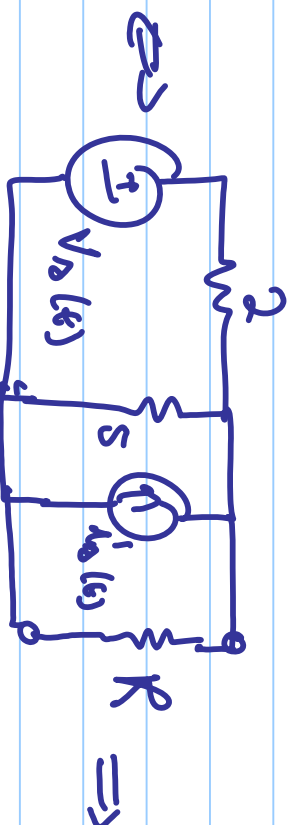
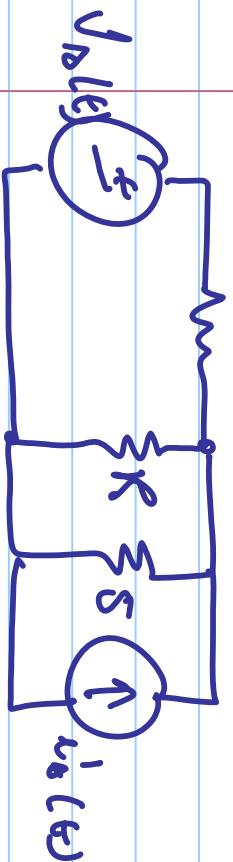


3.22

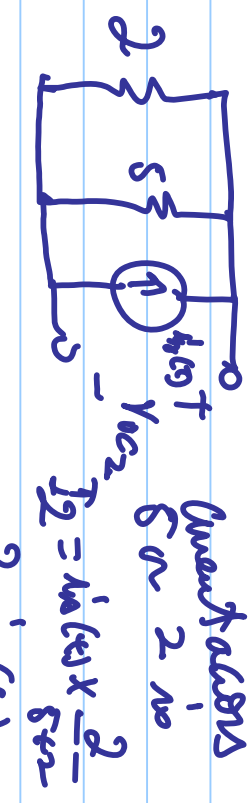

Using superposition method:

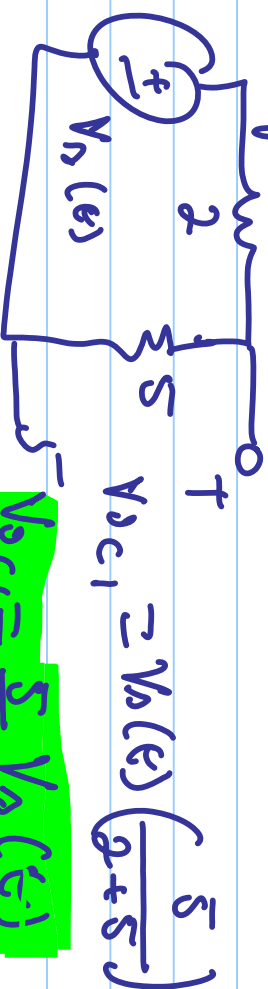① open circuit current  $I_{oc1} \Rightarrow$



② Short out the voltage source


$$V_{oc} = V_{oc1} + V_{oc2} =$$

$$V_{oc1} = \frac{S}{2} V_0(t)$$

$$\Rightarrow V_{oc2} = S \left( \frac{2}{7} \right) i_0'(t) =$$


Currents are  
6 or 2  $i_0'$   
 $I_2 = i_0'(t) \times \frac{2}{6+2}$

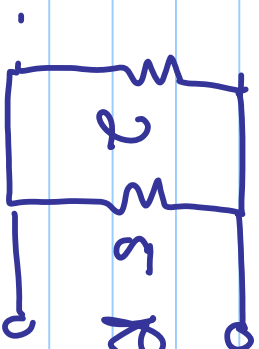$R_{th} \Rightarrow$  Short out Voltage & open circuit current




$$R_{th} = \frac{5 \times 2}{5+2} = \frac{10}{7} \Omega \Rightarrow$$


Thevenin's equivalent is

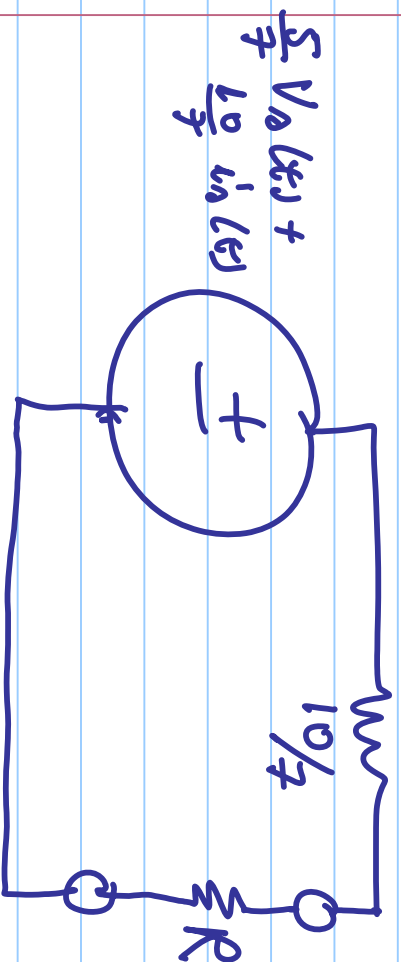

3.23

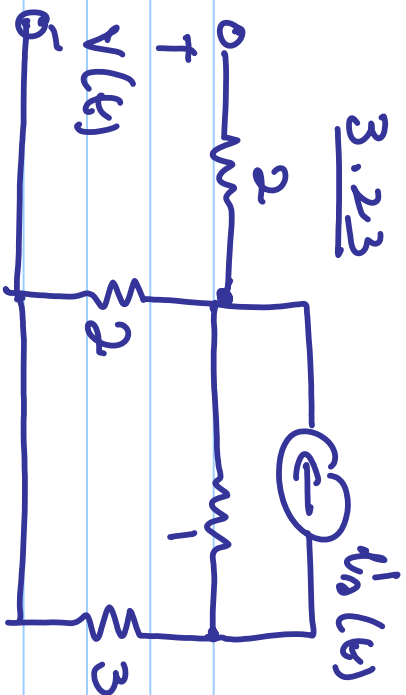

Use Source Transformation

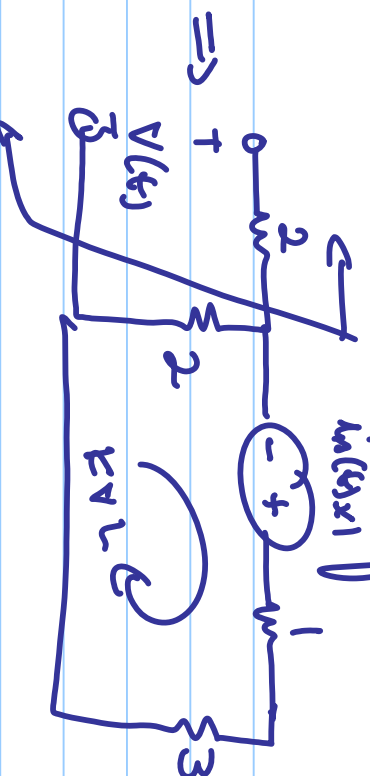

KVL:  $2I - i(t) + 3I + I = 0 \Rightarrow$

$6I = i(t) \Rightarrow I = \frac{i(t)}{6}$

$\Rightarrow$  the voltage across the  $2\Omega$  resistor

no  $V_{OC} = 2I = 2 \left( \frac{1}{6} i(t) \right) = \frac{1}{3} i(t)$


Thévenin voltage is  $V_{OC}$

Thévenin resistance is  $R_{Th}$

$R_{Th} = \frac{4 \times 2}{4 + 2} + 2 = \frac{8}{6} + 2 \Rightarrow$

$= \frac{8 + 12}{6} = \frac{20}{6} =$



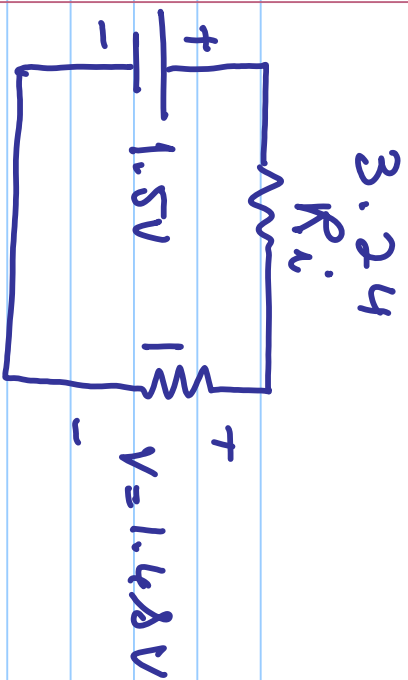

Using voltage divider  $\Rightarrow$


$$V = 1.5 \left( \frac{1}{1 + R_i} \right) \text{ where } V = 1.48V$$

$$\Rightarrow 1.48 = \frac{1.5}{1 + R_i} \Rightarrow (1 + R_i)(1.48) = 1.5V$$


$\Rightarrow$

[REDACTED]

### 3.25

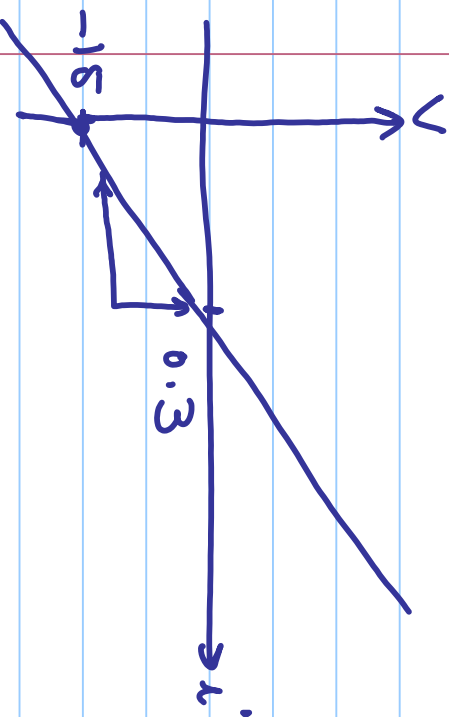



The Thévenin equivalent theorem is

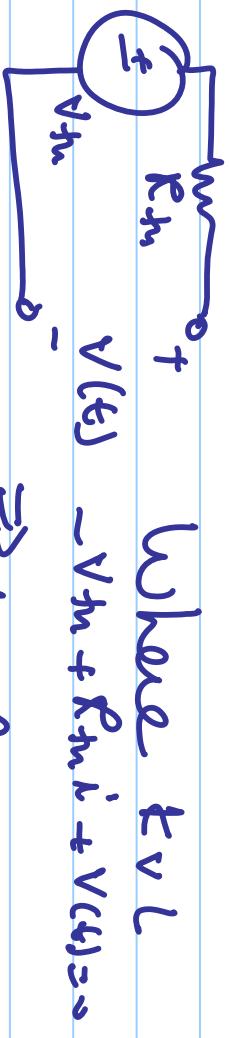


$$\Rightarrow \text{at } i = 0 \Rightarrow$$

$R_{th}$  is the Slope of the line

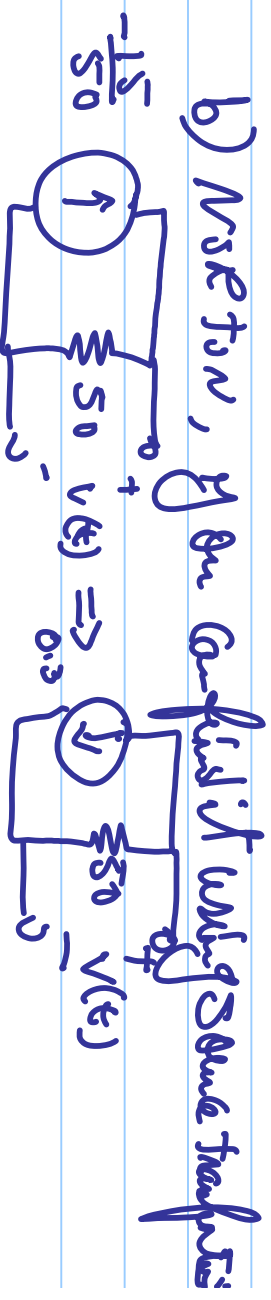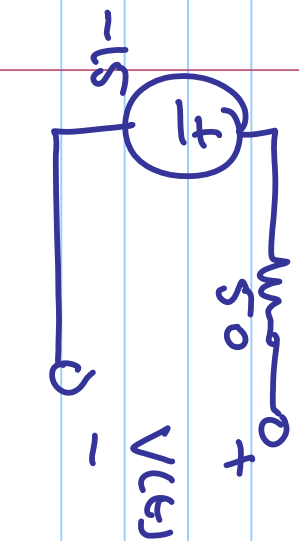
$$\therefore \text{the theorem: } \Rightarrow R_{th} = \frac{0 - (-15)}{0.3 - 0} = \frac{15}{0.3} = 50 \Omega = R_{th}$$



### 3.26

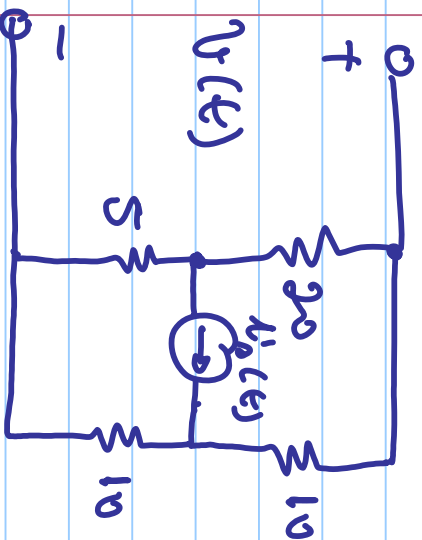

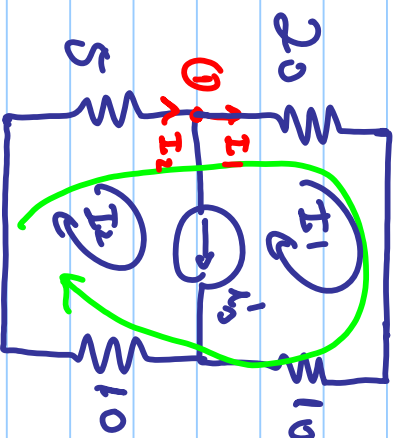we will go ahead & find  $V_{oc}$  & then find  $I_{sc}$ ...



@ node 1:  $I_2 = I_1 + I_A$

Super loop:

$$20I_1 + 10I_1 + 10I_2 + 5I_2 = 0$$

$$30I_1 + 15(I_1 + I_A) = 0$$

$$45I_1 = -15I_A \Rightarrow$$


$$I_1 = \frac{-15I_A}{45} = \frac{-1}{3}I_A$$

$$I_2 = I_1 + I_A = -\frac{1}{3}I_A + I_A = \frac{2}{3}I_A$$

$$\therefore V_{oc} = 20I_1 + 5I_2 = 20\left(\frac{-1}{3}I_A\right) + 5\left(\frac{2}{3}I_A\right) = 0$$

$$V_{oc} = \frac{20}{3}I_A + \frac{10}{3}I_A = \frac{10}{3}I_A$$


calculate  $R_{th}$ :

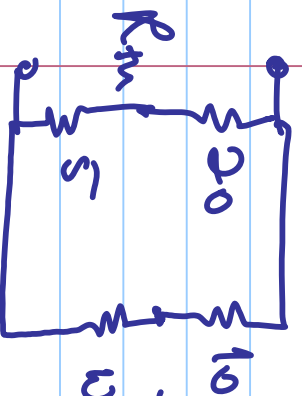


$$R_{th} = \frac{20 \times 20}{20 + 20} + 5$$

=

### 3.26 Continue

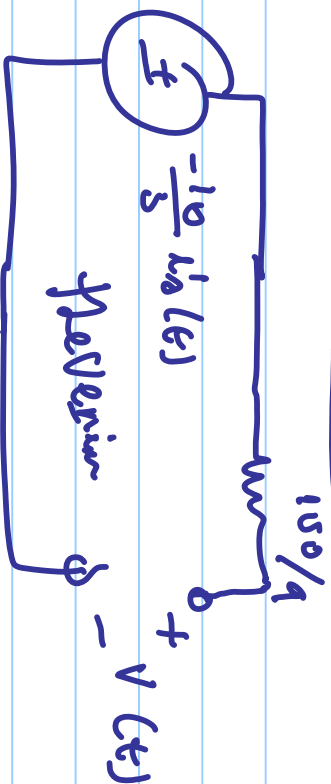


$\Rightarrow$  Norton:

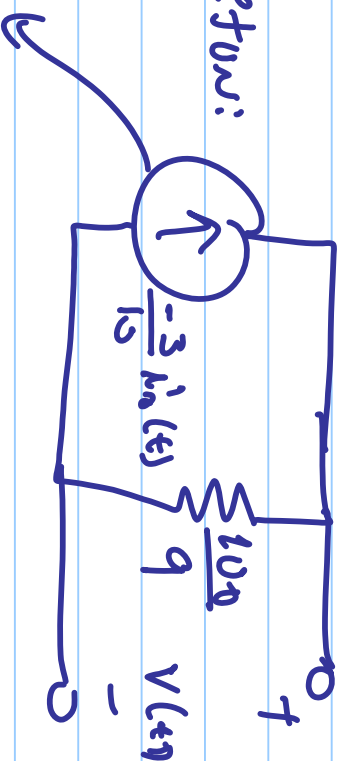

$$i_o(t) = \frac{V_o(t)}{R_{th}} = \frac{-\frac{10}{3}}{\frac{100}{9}} = -\frac{10}{8} \times \frac{9}{100} =$$

Note: the Book answer is  $-\frac{3}{10} i_o(t)$

P 3.28

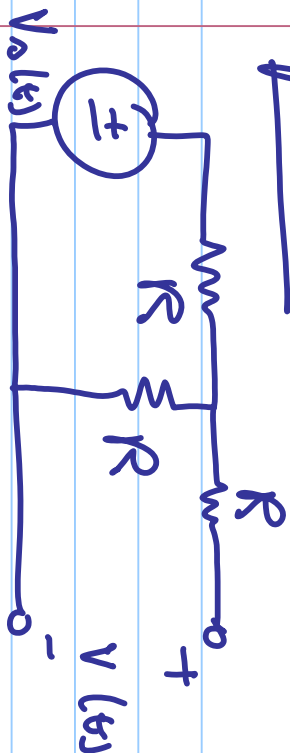


b) using source transfer  
 $\Rightarrow$  Norton:


$$a) V_{OC} = V_0(t) \frac{R}{R+R} = \frac{1}{2} V_0(t)$$

$$R_{th} = \frac{R \times R}{R+R} = \frac{R^2}{2R} = \frac{R}{2}$$
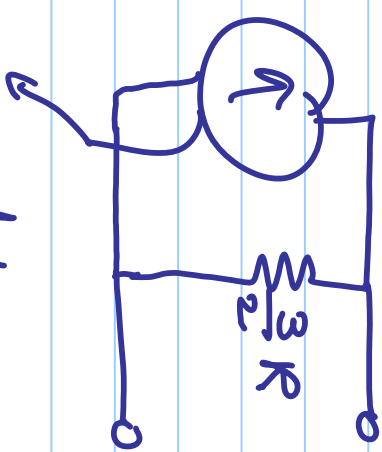
$$\therefore \frac{R}{2} + R = \frac{3}{2} R$$



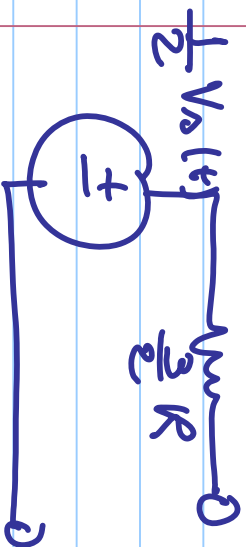
$$V_{OC} = \frac{\frac{1}{2} V_0}{\frac{3}{2} R} = \frac{1}{2} V_0 \times \frac{2}{3} R$$





3-41

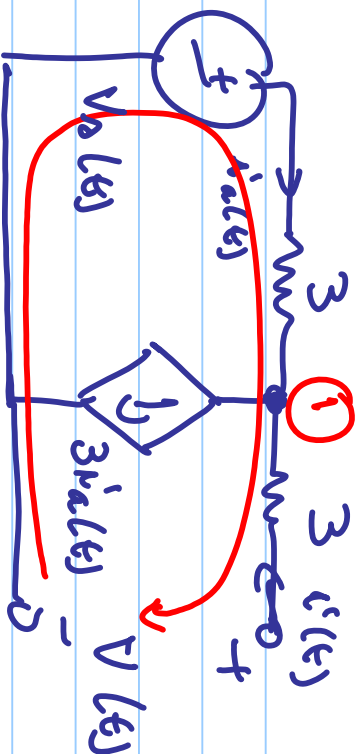

@ node 1 KCL:

$$i(t) = 3i_a(t) - i_a(t) = 2i_a(t)$$

$$\Rightarrow i_a(t) = \frac{1}{2} i(t)$$

Super loop  $\Rightarrow$


$$-v_a(t) + 3i_a(t) - 3i(t) - v(t) = 0$$

$$\Rightarrow v(t) = v_a(t) - 3\left(\frac{1}{2}i(t)\right) + 3i(t)$$


$$v(t) = v_a(t) + \frac{3}{2}i(t)$$

V-i Relation

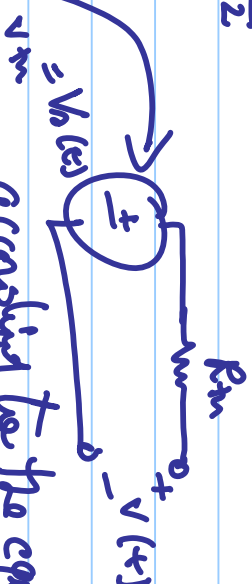
$$\Rightarrow v_a(t) = v_{th} \quad R_{th} = \frac{3}{2}$$



according to the equation  $\Rightarrow$

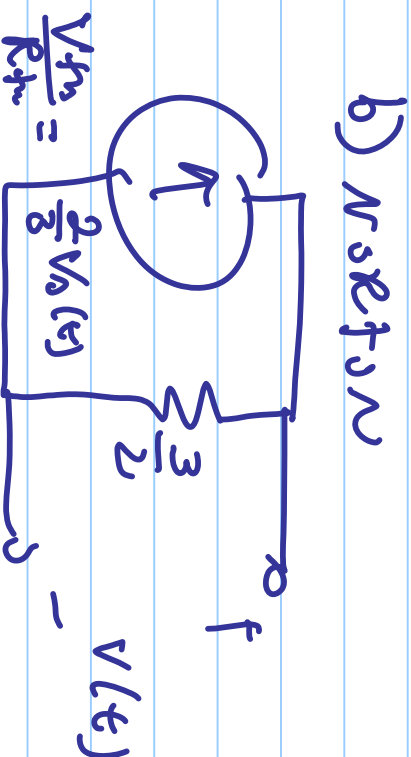

4.2

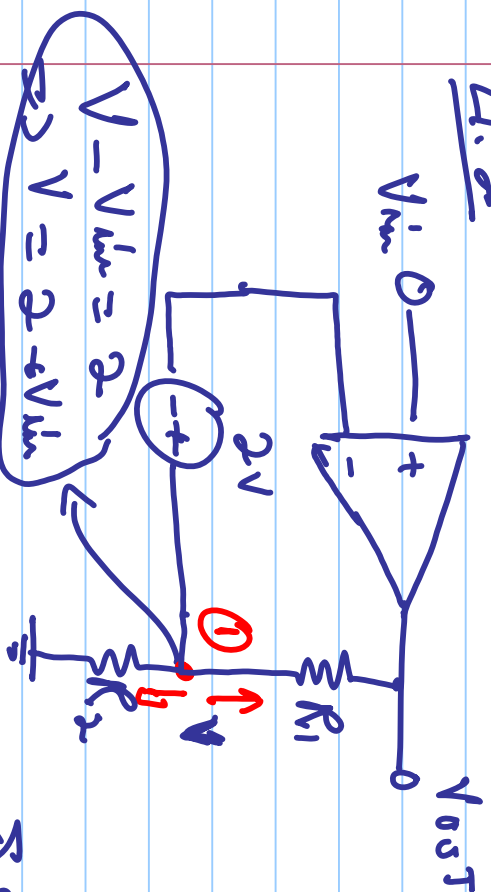

I deal op amp  $\Rightarrow$

$$V^- = V^+ = V_{in}$$

$$V^- = V^+ = 2$$

Solve for  $V_{out} \Rightarrow$

$$\frac{V - V_{out}}{R_1} + \frac{V}{R_2} = 0 \Rightarrow$$

$$\frac{2 + V_{in} - V_{out}}{R_1} + \frac{V_{in} + 2}{R_2} = 0$$

KCL @ node 1:


$$\frac{V_{out}}{R_1} = \frac{V_{in} + 2}{R_1} + \frac{V_{in} + 2}{R_2} \Rightarrow$$

$$\frac{V_{out}}{R_1} = \frac{R_2}{R_1} \frac{V_{in} + 2}{R_2} + \frac{R_1}{R_1 R_2} (V_{in} + 2) \Rightarrow$$

$$V_{out} = R_1^2 \frac{(V_{in} + 2)}{R_1 R_2} + \frac{R_1 R_2}{R_1 R_2} (V_{in} + 2) \Rightarrow$$

[Redacted]

4.4

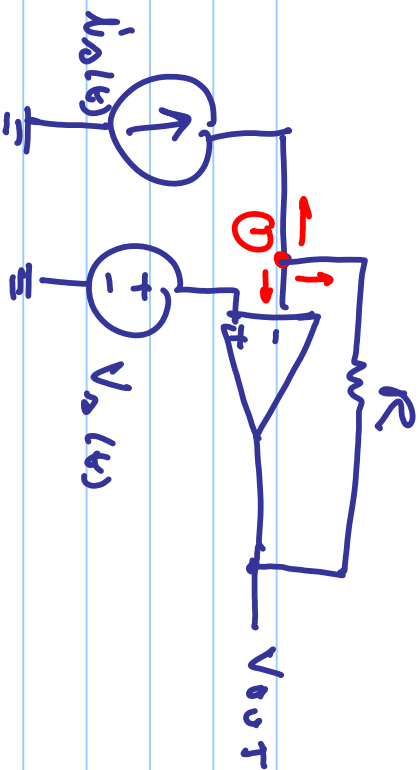

$$\frac{v_{out}}{R} = \frac{v_a(t)}{R} + i_a(t) \Rightarrow$$


[Redacted]

Ideal op amp  $\Rightarrow i^- = i^+ = 0$   
 $v^- = v^+ = v_a(t)$

KCL @ node 1  $\Rightarrow$

$$-i_a(t) + \frac{v_a(t) - v_{out}}{R} + i^+ = 0 \Rightarrow$$

Ex. 6

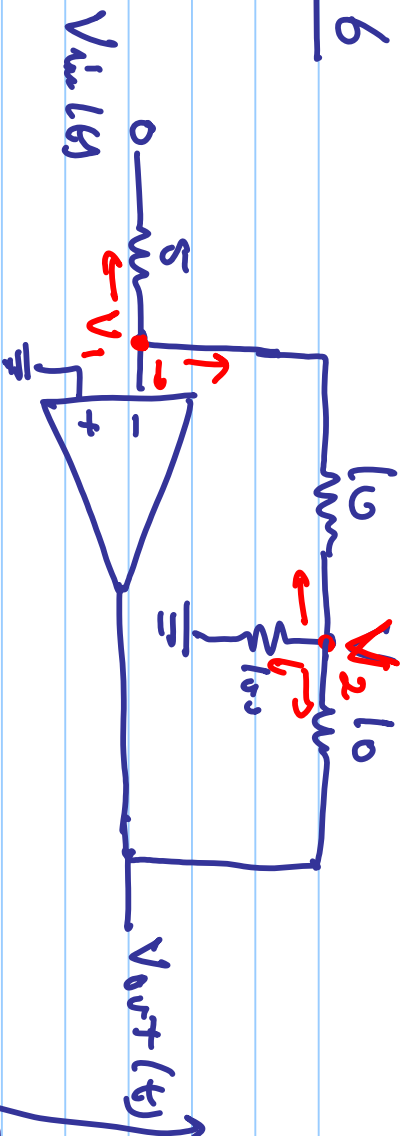

Ideal op amp:  $v^- = v^+ = 0$   
 $V^- = V^+ = 0$

We need 2 KCL

$$\text{at } V_1: \frac{V_1 - V_{in}}{l_0} + \frac{V_1 - V_2}{l_0} = 0$$

We know  $V_1 = V^- = V^+ = 0V$

$$\frac{-V_{in}}{l_0} - \frac{V_2}{l_0} = 0 \Rightarrow$$

$$\boxed{-2V_{in} = V_2}$$

at  $V_2$ :

$$\frac{V_2 - V_1}{l_0} + \frac{V_2 - V_2}{l_0} = \frac{V_{out}}{l_0}$$

$$V_2 \left( \frac{1}{l_0} + \frac{1}{l_0} + \frac{1}{l_0} \right) = \frac{V_{out}}{l_0}$$


$$V_2 \left( \frac{3}{l_0} \right) = \frac{V_{out}}{l_0} \Rightarrow$$

$$V_2 \left( \frac{3}{l_0} \right) = \frac{V_{out}}{l_0} \Rightarrow$$

$$V_{out} = 3V_2 \Rightarrow$$

[Redacted]

4.14

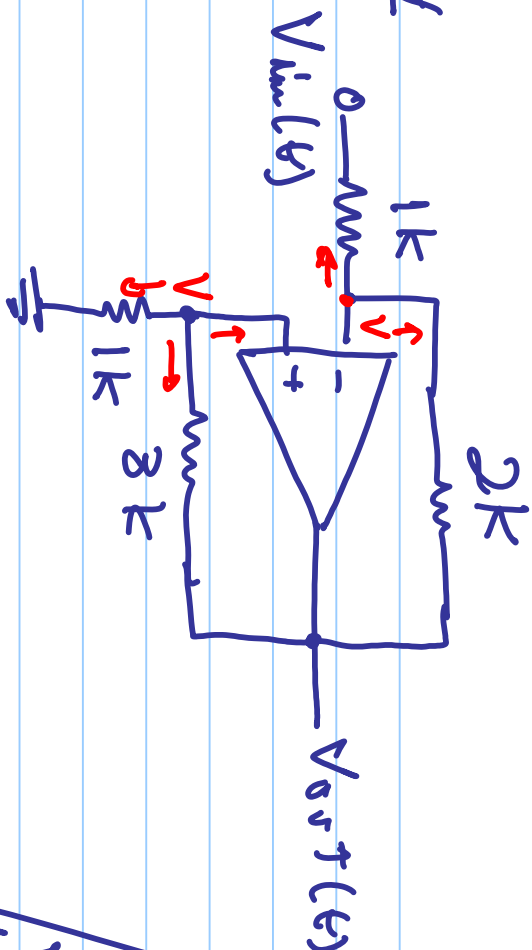

$$3V - V_{out} = 2V_{in} \Rightarrow \frac{3V - V_{out}}{3} = 2V_{in} \quad (1)$$

$$KCL @ V^- \Rightarrow \frac{V - V_{out}}{3k} + \frac{V}{1k} = 0 \Rightarrow$$

$$V\left(\frac{1}{3} + 1\right) = \frac{V_{out}}{3} \Rightarrow \frac{4}{3}V = \frac{V_{out}}{3} \Rightarrow V = \frac{V_{out}}{4} \quad (2)$$

equating equations 1 & 2  $\Rightarrow$

$$\frac{V_{out}}{4} = \frac{2V_{in} - V_{out}}{3} \Rightarrow$$

$$3V_{out} - 4V_{out} = 8V_{in} \Rightarrow$$

$$\Rightarrow V_{out} = -8V_{in}$$

$$Ideal op amp \Rightarrow i^- = i^+ = 0$$

$$V^- = V^+$$

$$KCL @ node V^- \Rightarrow$$

$$\frac{V - V_{in}(t)}{1k} + \frac{V - V_{out}}{3k} + i^- = 0$$

$$V\left(1 + \frac{1}{3}\right) - \frac{1}{3}V_{out} = V_{in} \Rightarrow$$